

BOURNS[®]

Circuit Protection Products

TBU[™] Products Application



Overview

- **Founded in 1947, Bourns, Inc. is a leading provider of components and solutions for Motion Control, Circuit Protection and Circuit Conditioning**
- **Privately held company headquartered in Riverside, California**
- **Approximately 4200 employees with 12 worldwide manufacturing centers for electronic products**
- **All manufacturing centers are ISO 9001 and/or TS16949 certified**




Levels of Protection

- **The TBU solution provides a higher level of protection**


- High Energy Surge Protection

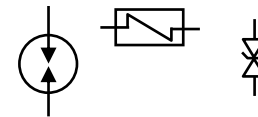- ◆ Provides resistibility against lightning and power induced faults



- Moderate Energy Surge Protection

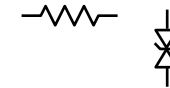- ◆ Typically need to add components to increase energy resistibility




- Low Energy Surge Protection

- ◆ Basic ESD protection if IC structures are not adequate




- Protected IC

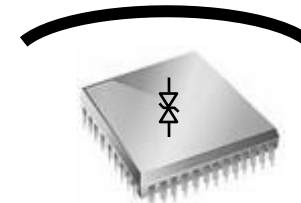- ◆ Sometimes contains sufficient protection inside the chip for low energy surges



Bourns® Protection Device


Multifuse®

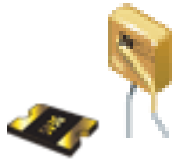


CPTC



Telefuse™

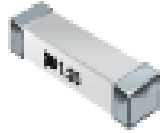

SinglFuse™

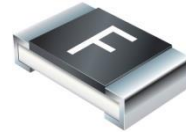

Over Current Protection


Over Voltage Protection



LSP



TBU™

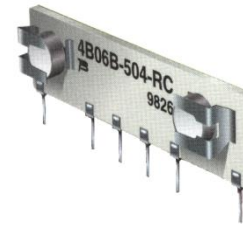

LPM

Magnetics



MOV




GDT



TISP®



TVS

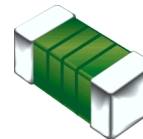

Chip Guard®




TCS™





OSP

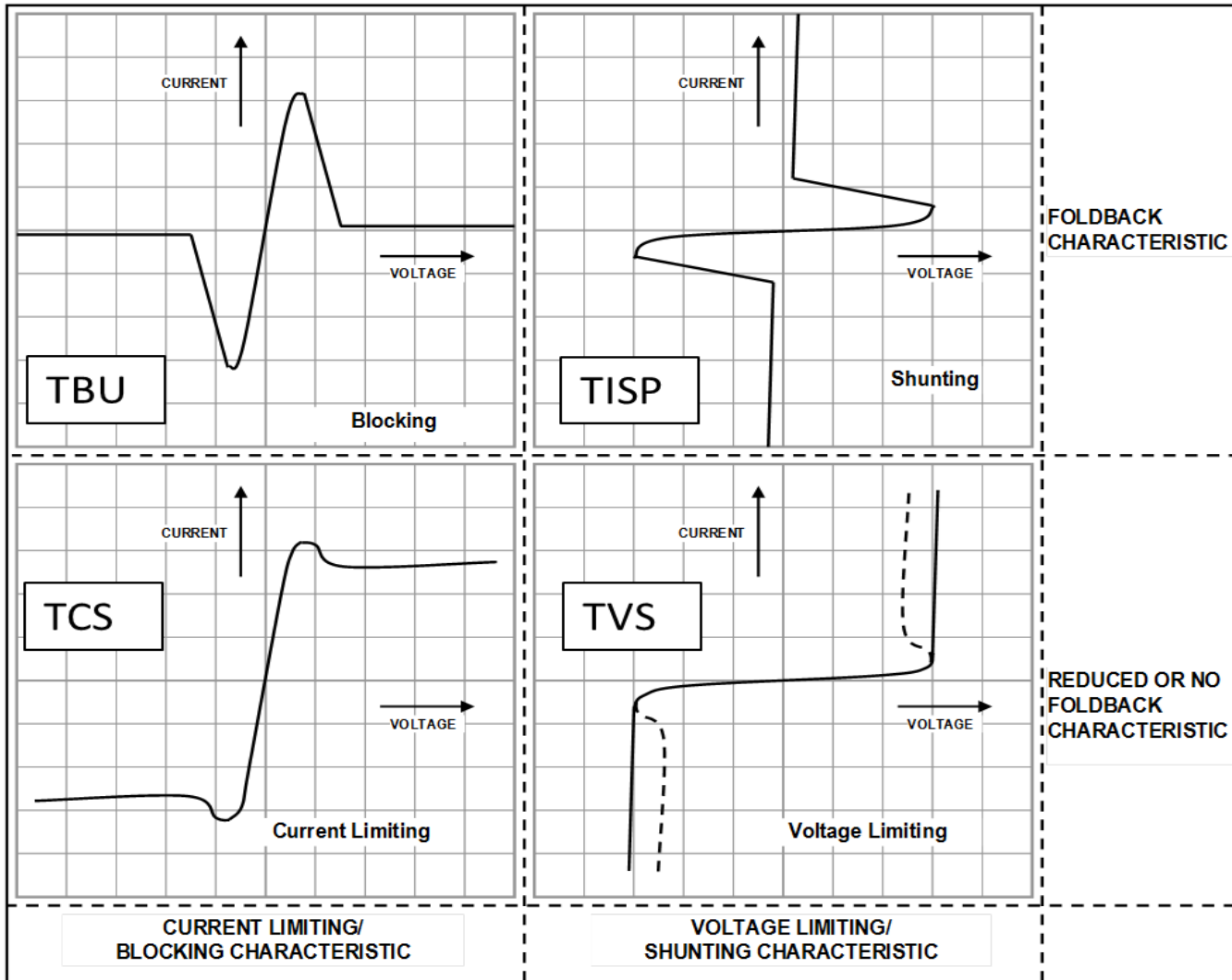General Characteristics of the Device Types




I-V Characteristic of a TBU™ device

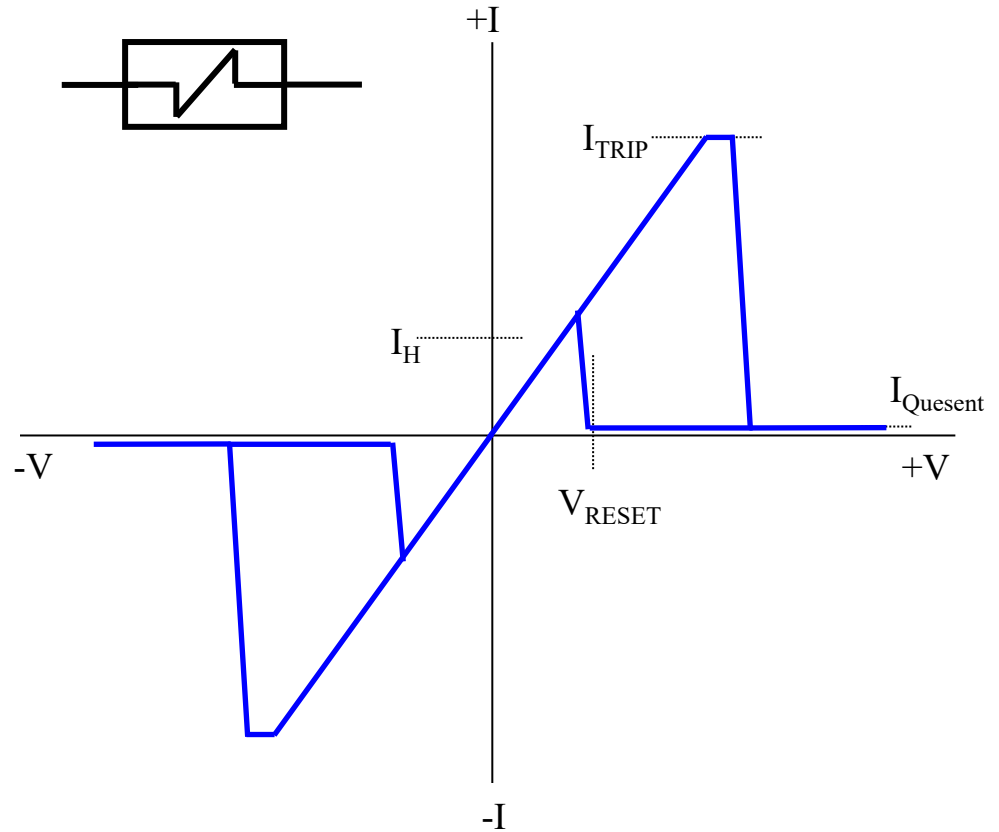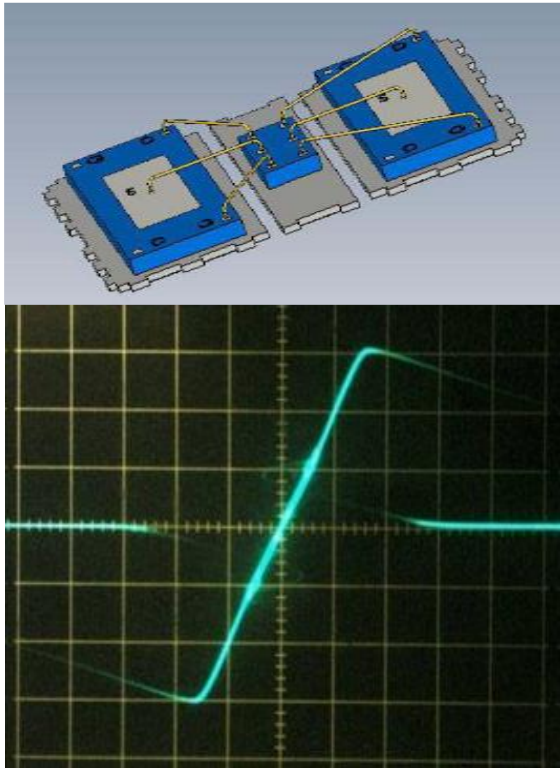- Below trigger threshold, TBU device acts like a resistor
- Above trigger threshold, TBU acts like a $\sim 1\text{mA}$ current source



Conventional Protection Solution


Lightning test circuit

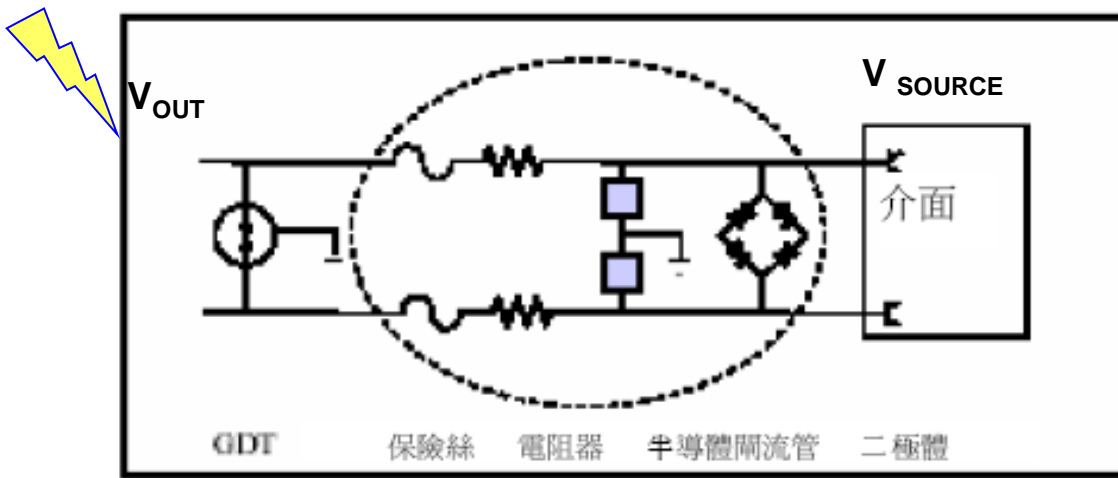


- Circled parts indicating the secondary protection and the Coordinating impedances.

Example: OVP Coordination using a TBU™ device

Lightning test circuit

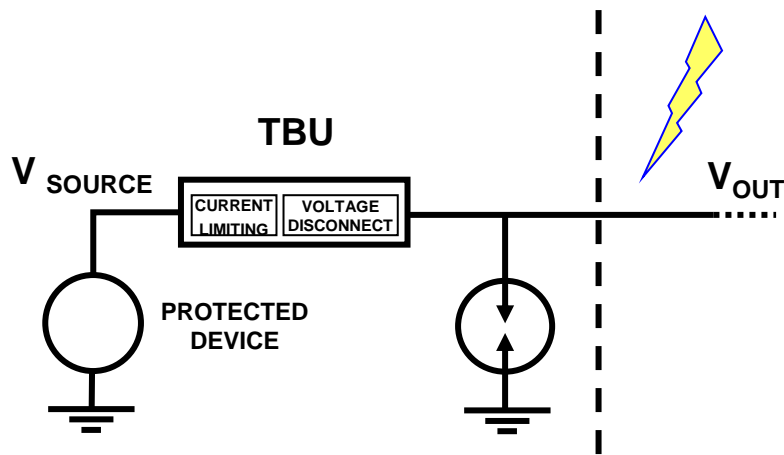


Surge 5000V, 1/50 μ sec

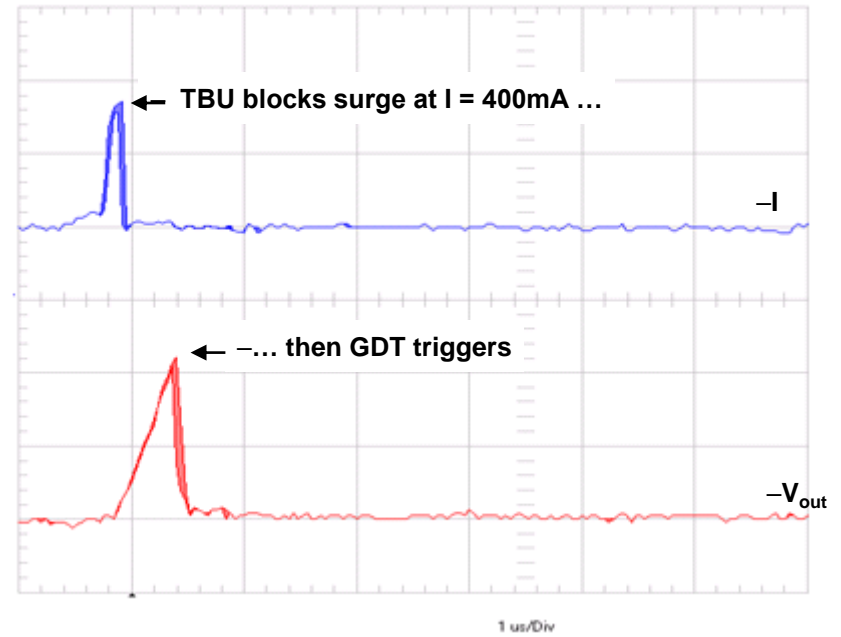

TBU Advantages & Benefits


Example: RS485 Port Protection

TVS/Resistor Solution

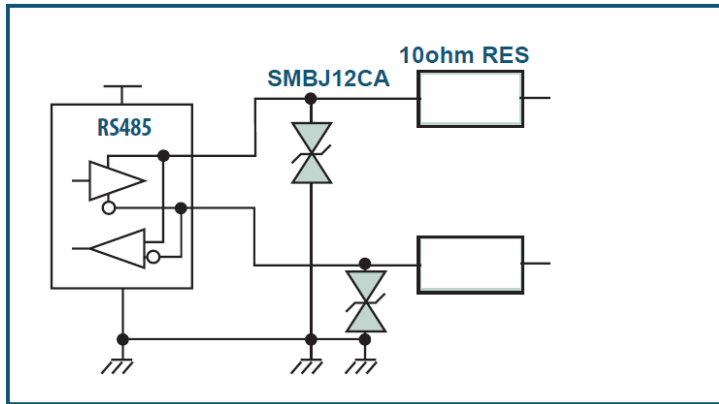

- Limited Surge Protection
- No AC Power Cross protection
- Non-Resettable
- Fulfills lower tier of protection envelope

TBU solution

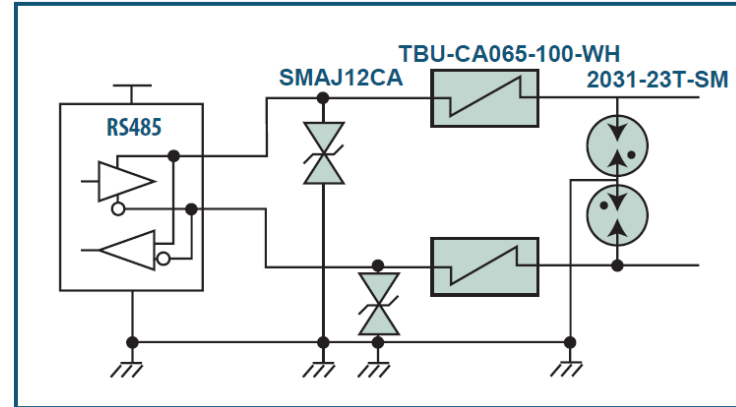

- High energy surge protection
- Power cross protection
- Resettable solution
- Works irrespective of surge duration or rate-of-repetition
- No let-thru energy to sensitive chipsets
- Wide operational bandwidth

RS-485 Port Protection Evaluation Board For TBU Solution

Figure 1: RS-485 Evaluation Board Schematic

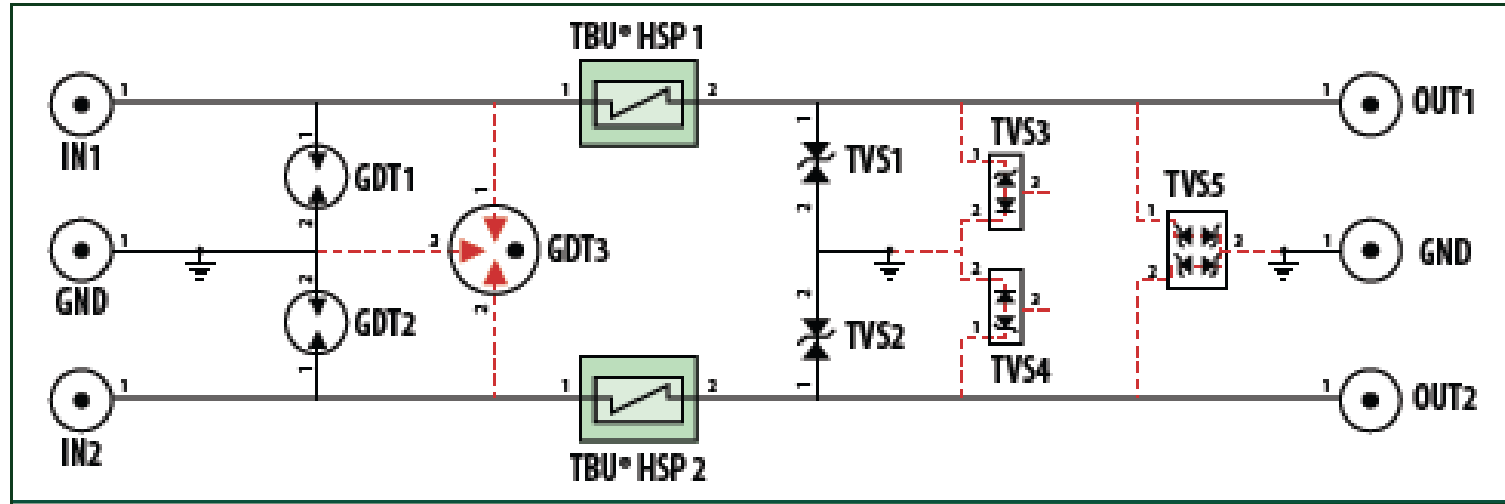


Figure 2: RS-485 Evaluation Board 1


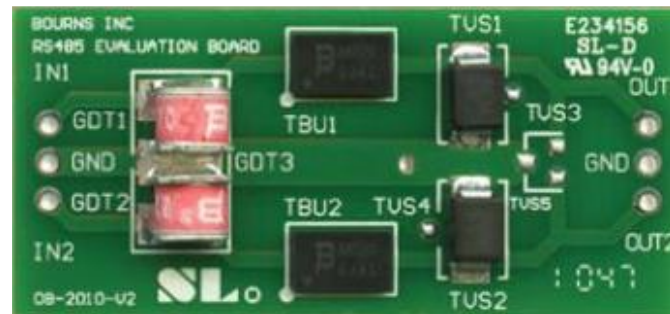


Figure 3: RS-485 Evaluation Board 2

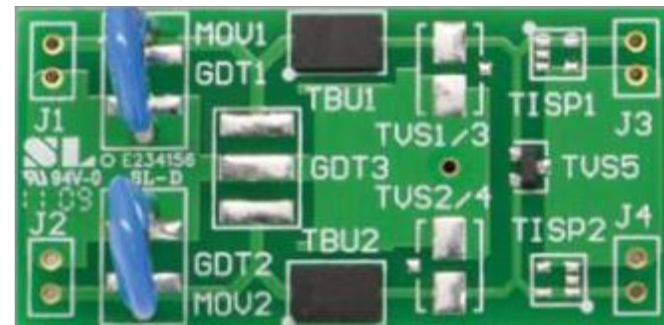

ADI RS-485 Evaluation Board

Features:

- Cost-efficient, three panel board
- Tests circuits at the beginning of the design cycle
- Use of schematics and layout as a starting point in your design
- Certified to protect ADI's ADM3485E, 3.3 V RS-485 transceiver for:
 - 6 kV, 4 kV and 1 kV Surge (IEC 61000-4-5)
 - 15 kV Air Discharge ESD (IEC 61000-4-2)
 - 2 kV EFT and 8 kV Contact (IEC 61000-4-4)
- The ezLINX™ iCoupler® Isolated Interface Development Environment

For more information:

- Visit http://www.bourns.com/adi_board
- Register to watch the webcast, [Safeguarding RS485 Communication Networks from Harmful EMC Events](#), on March 27, 2013


The evaluation boards are now available through select authorized distributors of Bourns and ADI.

Should you have any questions or need additional information, please contact [Bourns Customer Service/Inside Sales](#) or [ADI Technical Support](#).



LVDS Protection

- TBU devices have been evaluated and recommended by National Semiconductor for LVDS applications
 - u Tested to 3 Gbps up to 100 meters

 **National Semiconductor**
The Sight & Sound of Information


www.national.com

Signal Integrity Evaluation of Bourns Lightning Protection Solutions

Bourns lightning protection solutions suitable for National Semiconductor's high speed interface devices consist of gas discharge tubes (GDT) and transient blocking unit (TBU™) protectors. Table 1 summarizes common lightning protection standards in the industry and Bourns devices suitable for each of the standards.

| | GR-1089 Intra-B | GR-1089 Intra-B Enhanced | IEC61000-4-5 Class 0-3 | IEC61000-4-5 Class 4-5 | ITU-T K.21 |
|--------------------|-------------------------------------|--------------------------------|---------------------------|---------------------------|------------|
| Lightning | 800V/100A Diff 1500V/100A Com | 5000V/500A | 2000V/48A | 4000V/95A | 6000V/150A |
| Power Cross | 120V | 230V | - | - | 230V |
| TBU | C650 | C850 | C650 | C850 | C850 |
| GDT | G5500AS | G5200AS | G5500AS | G5200AS | G5200AS |
| Resistance | 10Ω | 14Ω | 10Ω | 14Ω | 14Ω |
| Capacitance | 1 pF | 1 pF | 1 pF | 1 pF | 1 pF |

Table 1. Common Lightning Protection Standards and Recommended Bourns Solutions

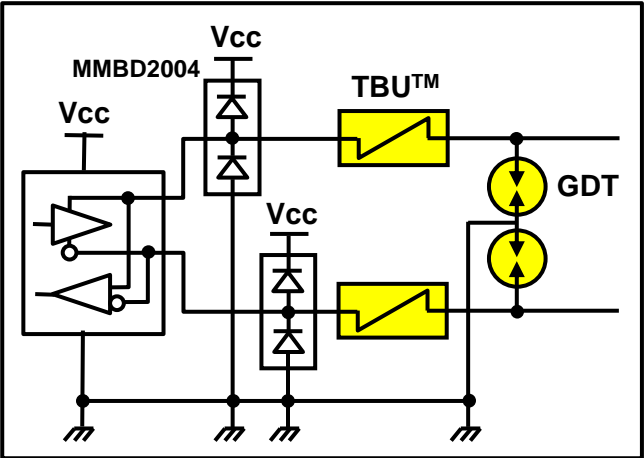


◆ TBU and GDT device selection are per the required protection level

Excerpt from National Semiconductor white paper

TBU-CA Solution for RS485


Lightning: 8/20 μ s, 20kV, 10kA

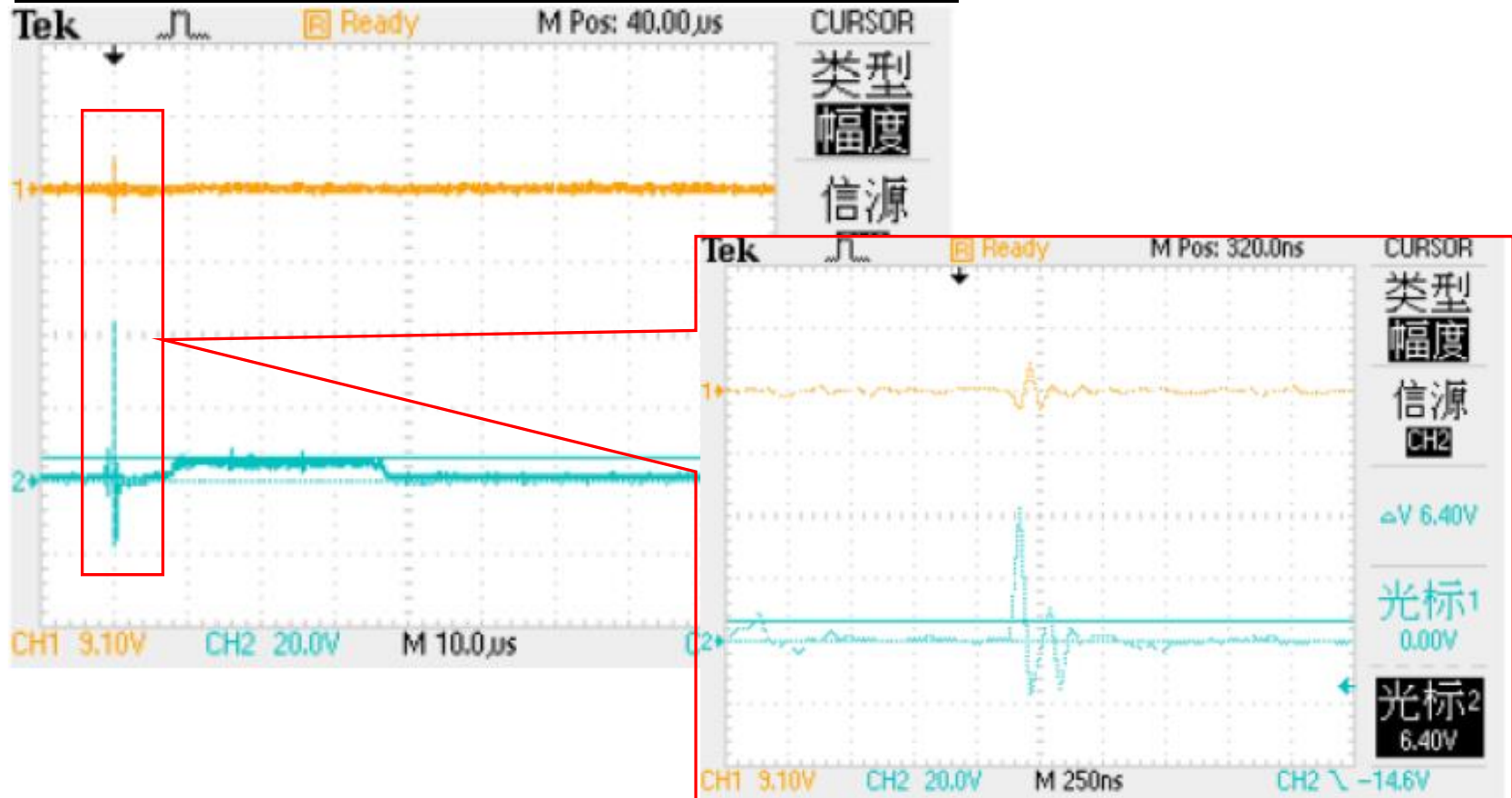


Conventional Vedio Protection Solution

——(GDT+PR+TVS)

Lightning: 8/20 μ s, 20kV, 10kA

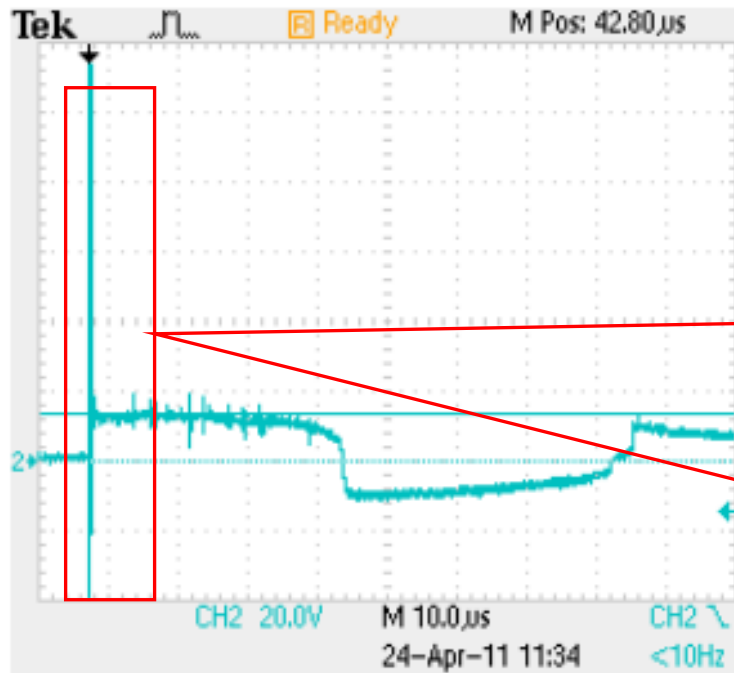


TDS 2012B - 11:38:59 2011-4-24

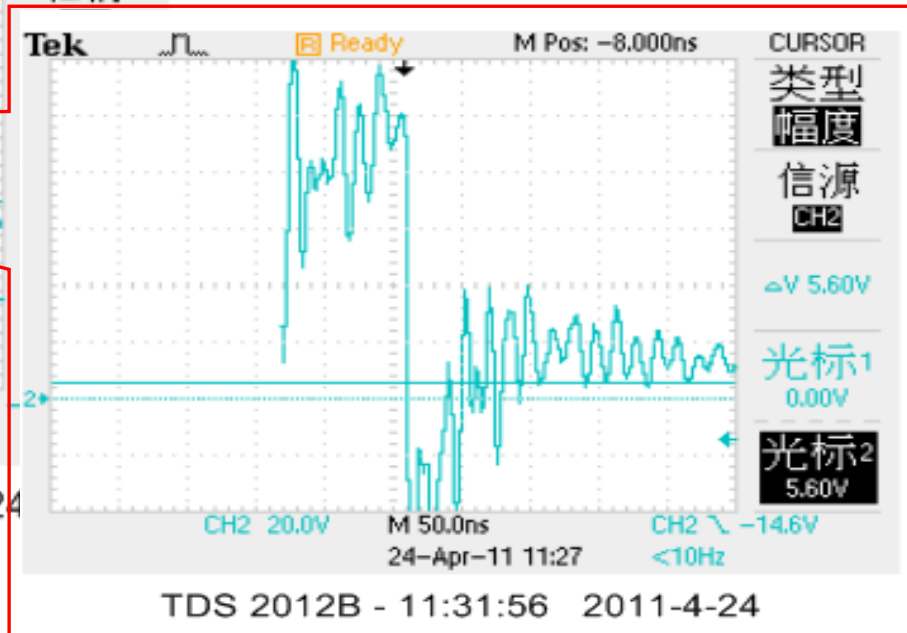


TDS 2012B - 11:31:56 2011-4-24

Leading Technology-Integrated MDF Modules




2410

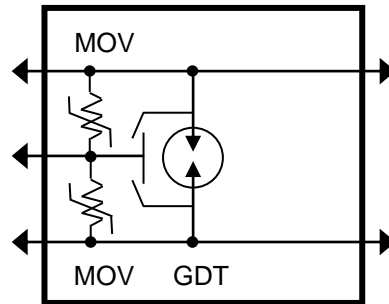

2430

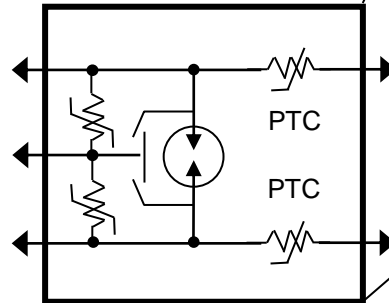


2470

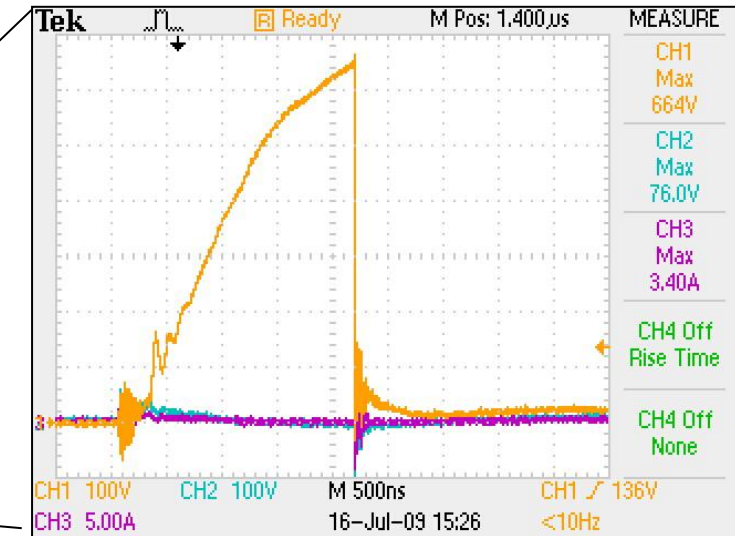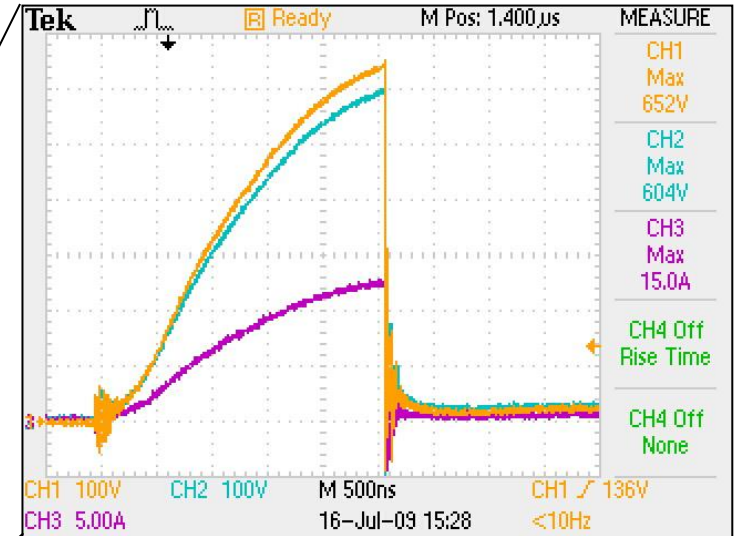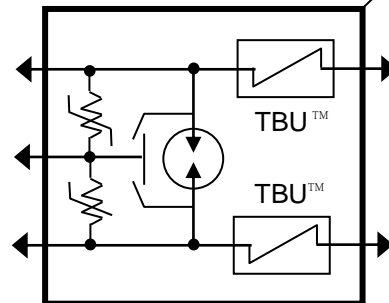

AC Power Cross using a TBU™ device

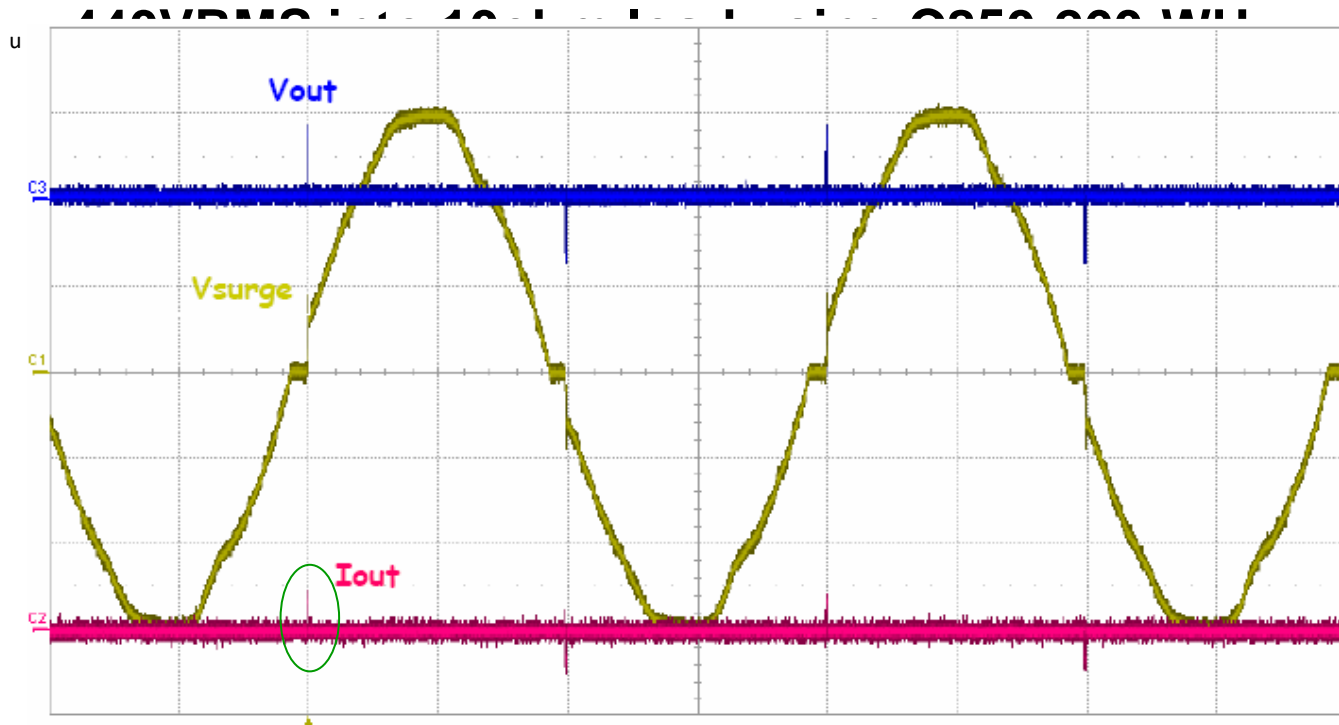- During power cross, the TBU device turns on and off every cycle:




V_{SURGE} : 100V/div 5ms/div
 I_{OUT} : 1A/div 5ms/div
 V_{OUT} : 5V/div 5ms/div

V_{out} determined by the load resistance
and TBU trip current:

$$V_{out} = I_{out} * R_{load}$$


Bandwidth using a TBU™ device

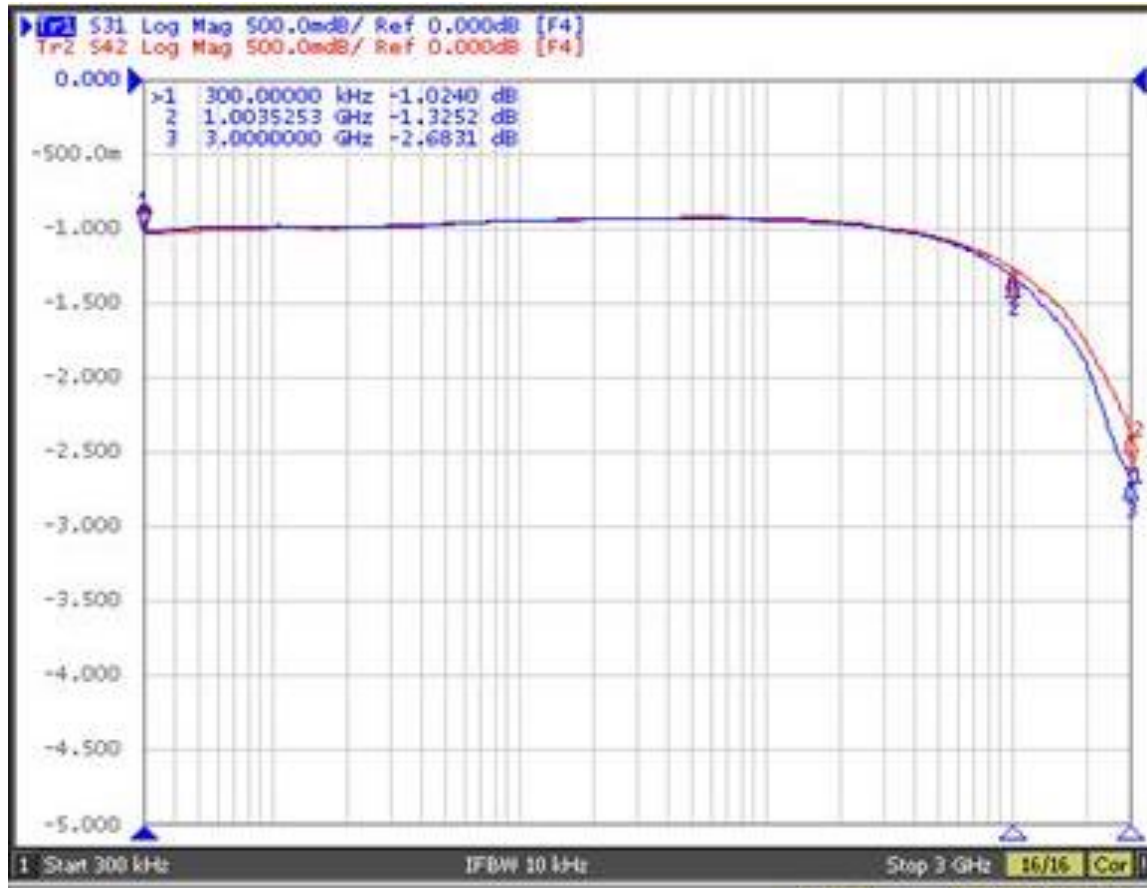- Insertion Loss of two C850-260-WH TBU devices in a 50ohm LVDS test circuit




TBU-CA Solution for RS485

传输特性图 (T=25°C, 0.3-20MHz)

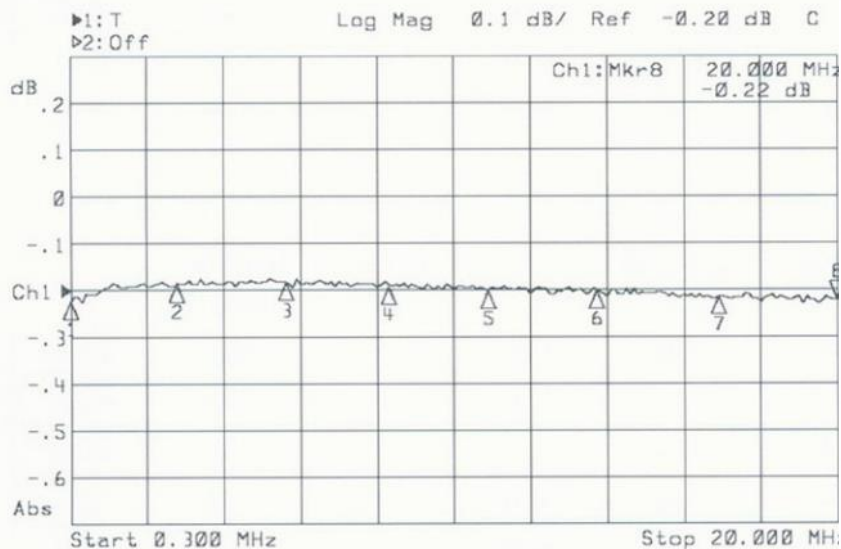

温度特性图 (20°C-80°C, 20MHz)



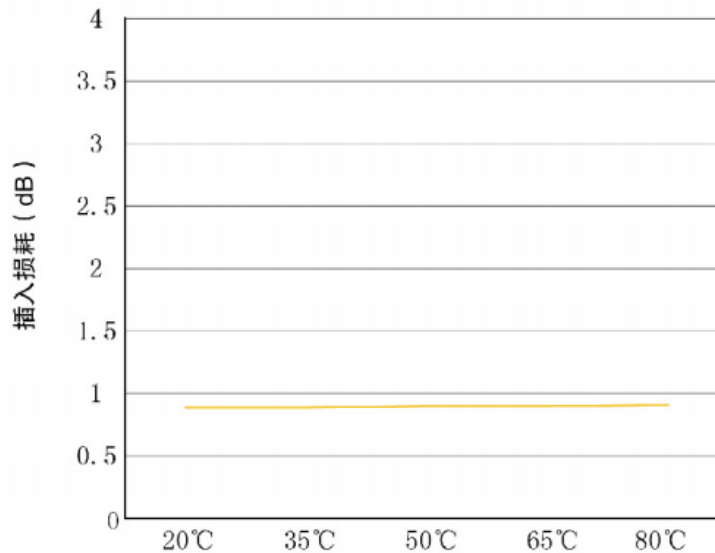


20MHz下的温度影响



TBU Has Exceptional Stability

Fault cycle test results (UL1434)

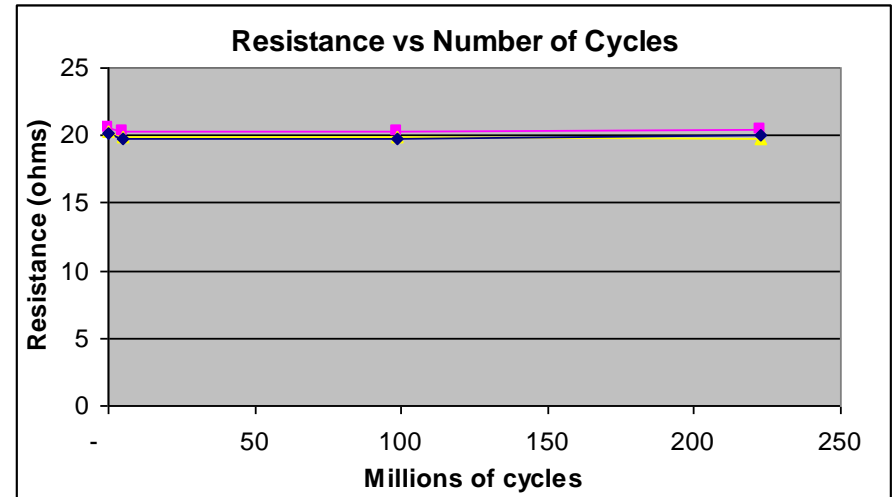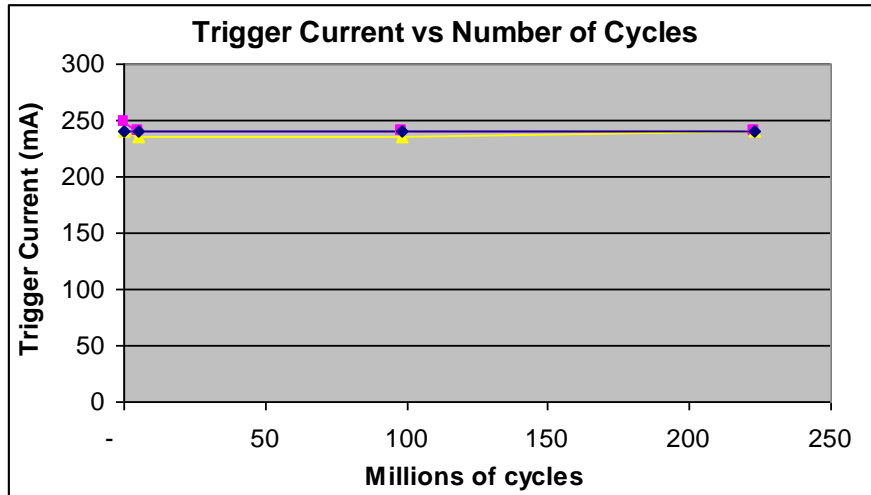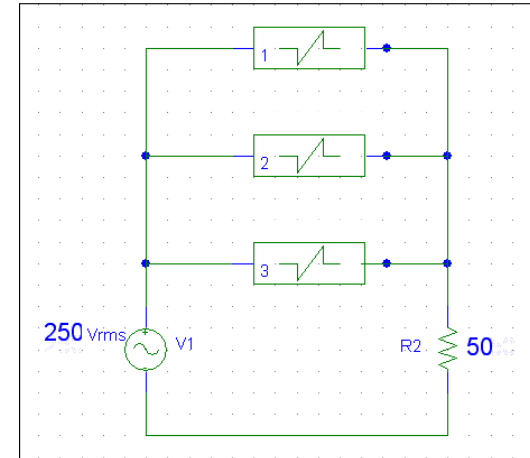
- 250V_{ac}, ~4A fault current, 85° C;
- TBU remains unchanged after 200M cycles



常规500V隔离应用电路图

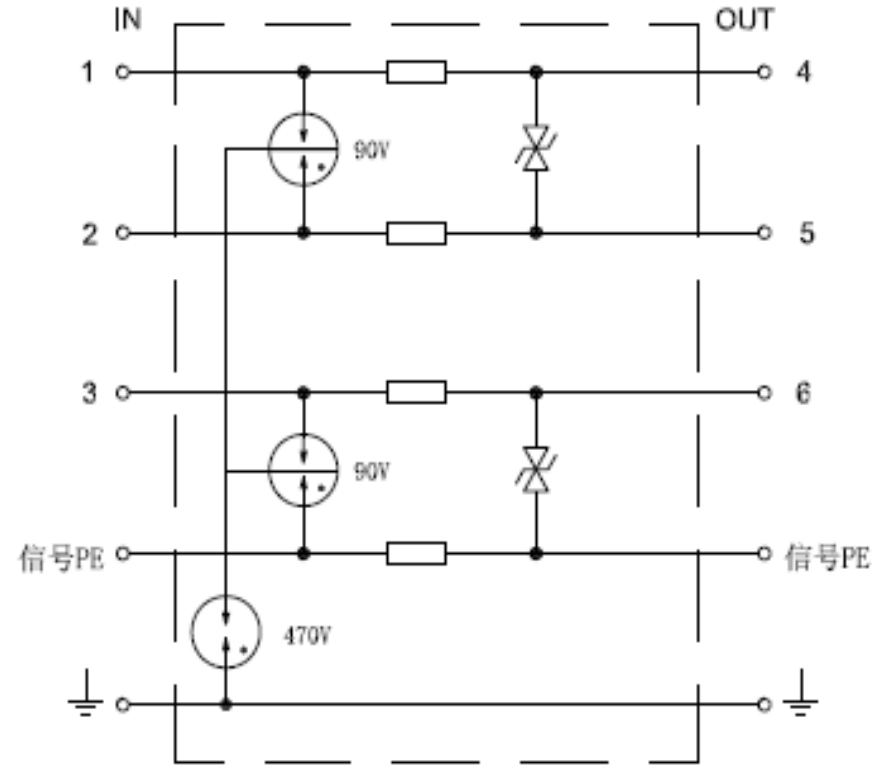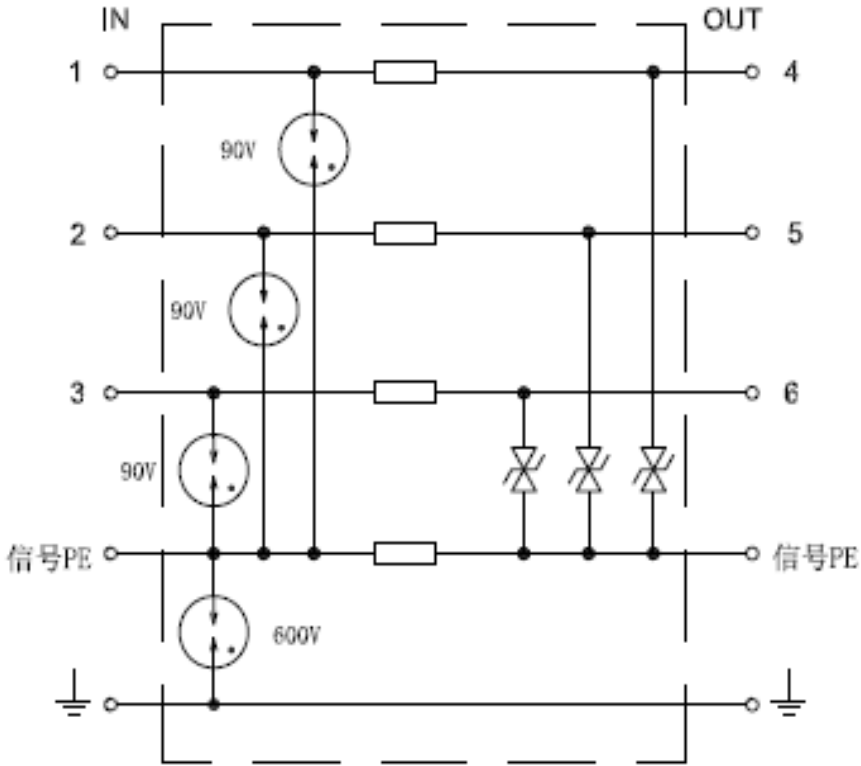

RS485+RS232复合端口加强浪涌保护方案 (500V隔离)

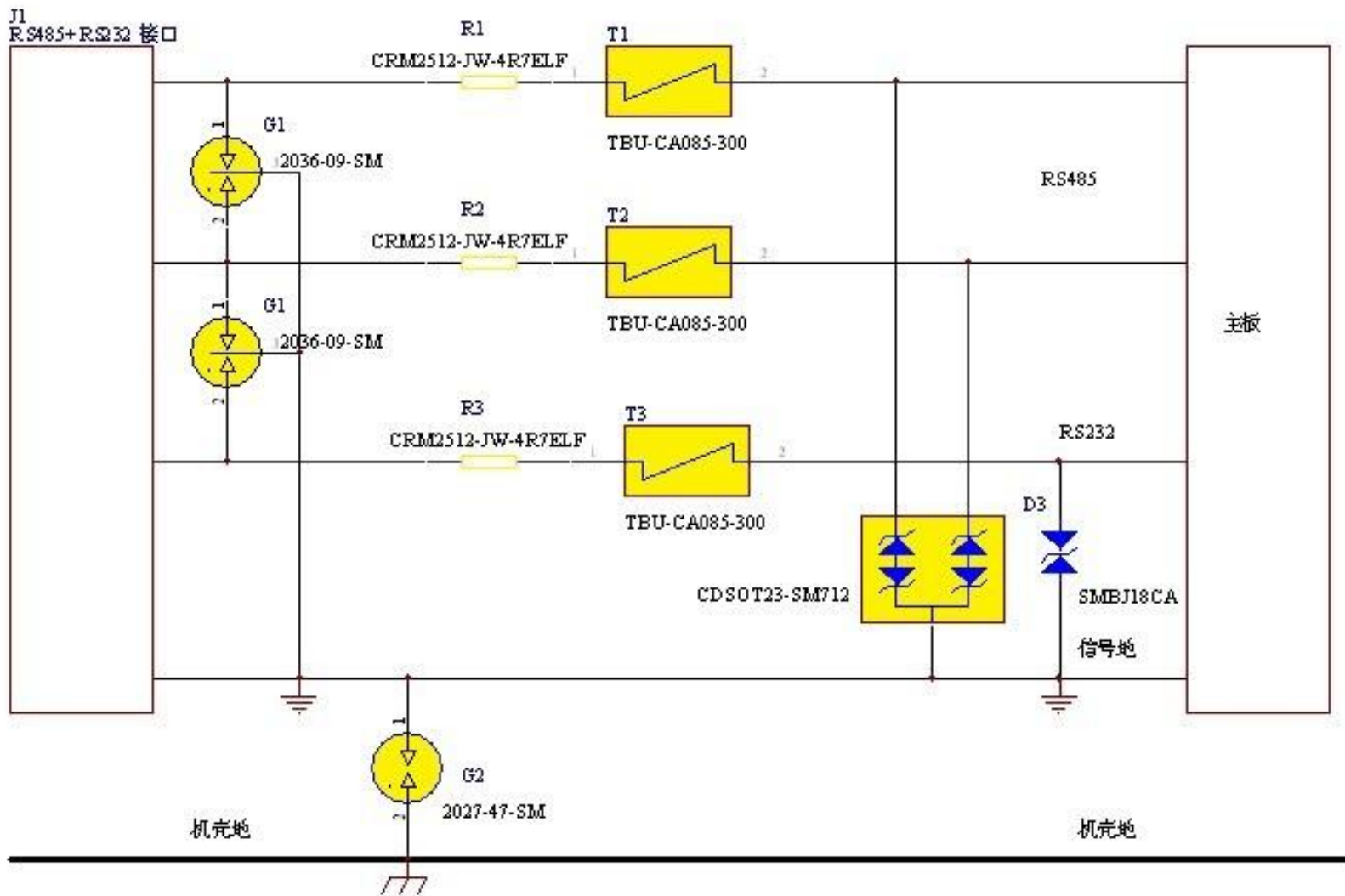

8/20 us 10KV/5KA浪涌冲击 & 500V绝缘耐压测试

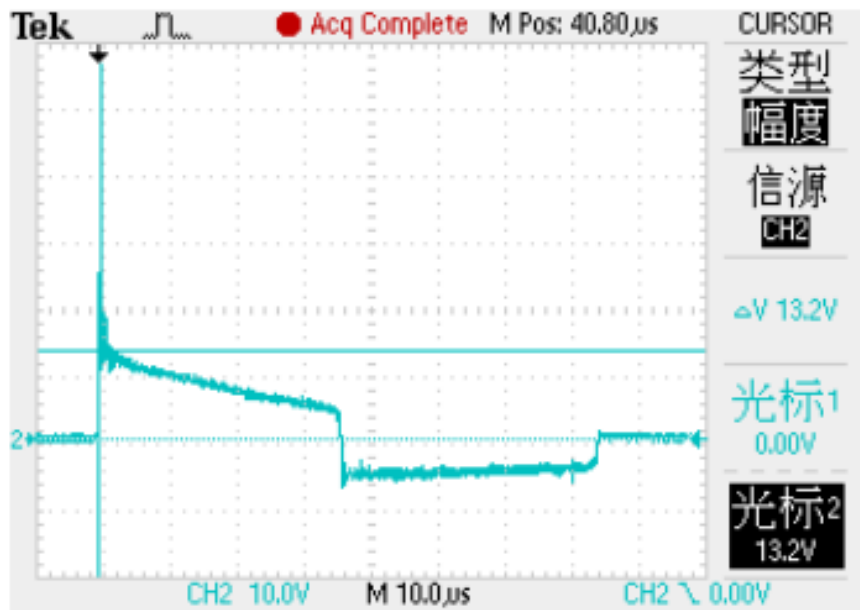


图1: L-L信号到信号地实测残压图

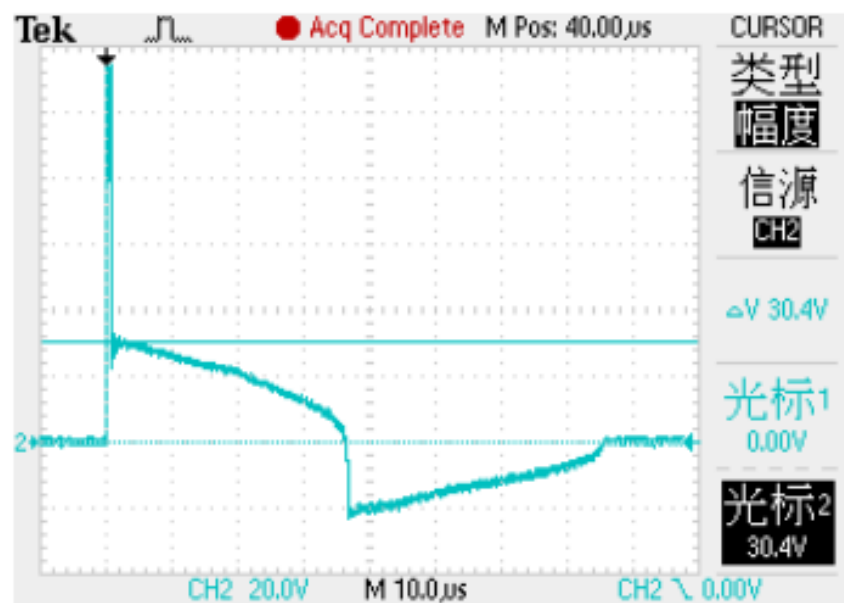



图2: L-PE信号到机壳地实测的残压图

PS: CDSOT23-SM712的正向击穿启动电压为13.3V,反向击穿启动电压为 $7.5V \times 2 = 15V$.
因为后端有18V的TVS做钳位,所以信号地上的残压不会很高.

Serial Port Protection Solution

Current Solution: 2*TVS+2*PPTC


Next Solution: P40-G240-WH

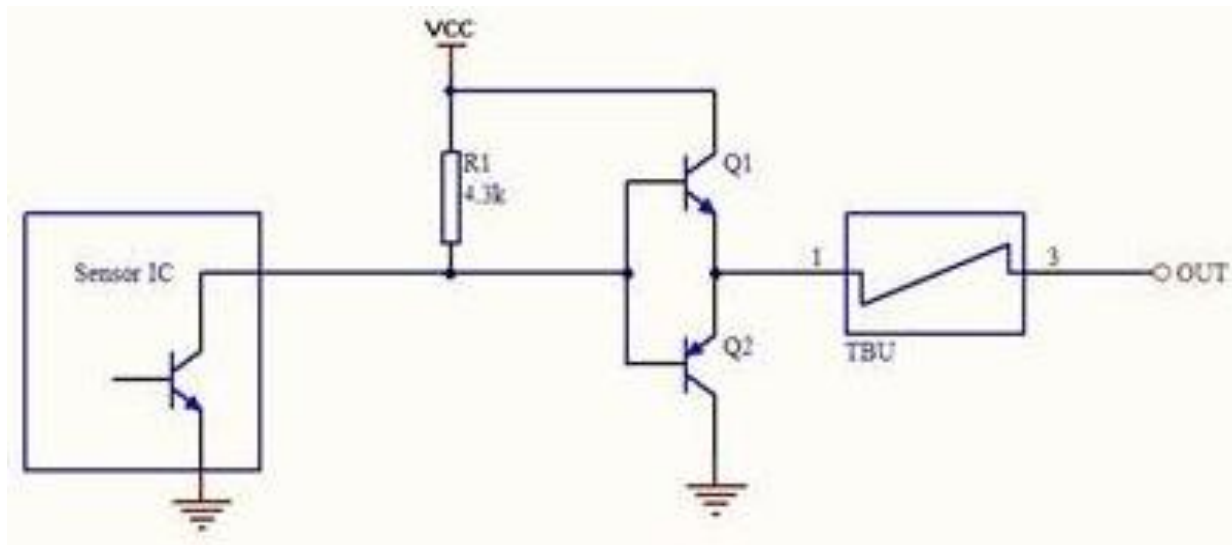


Application: IC's operation voltage is 5V and need pass 12V DC power cross testing

TBU Advantages: High reliability, it can work in a wide range of temperature; Fast response time, the output residual depression and small package size

4~20mA软启动应用电路图

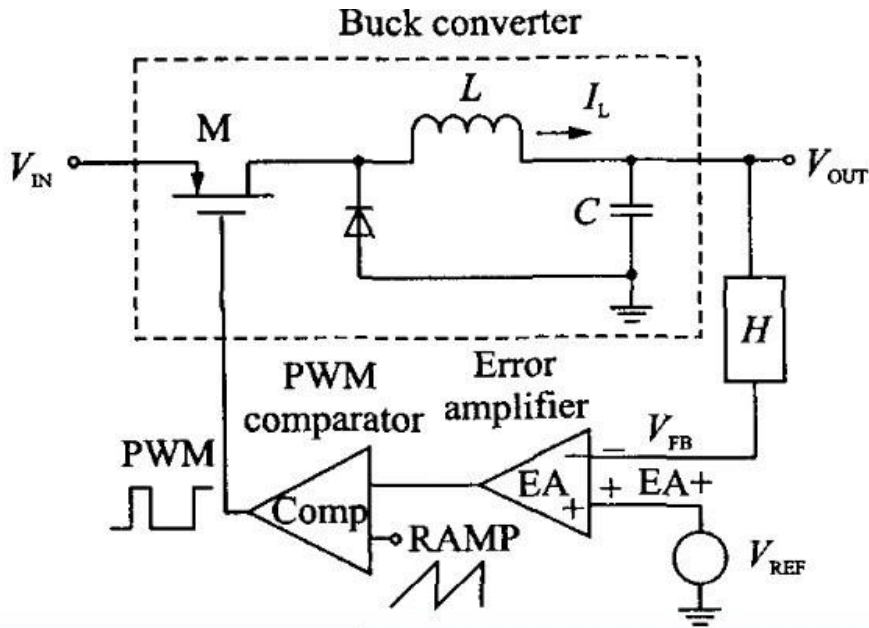



传统软启动电路

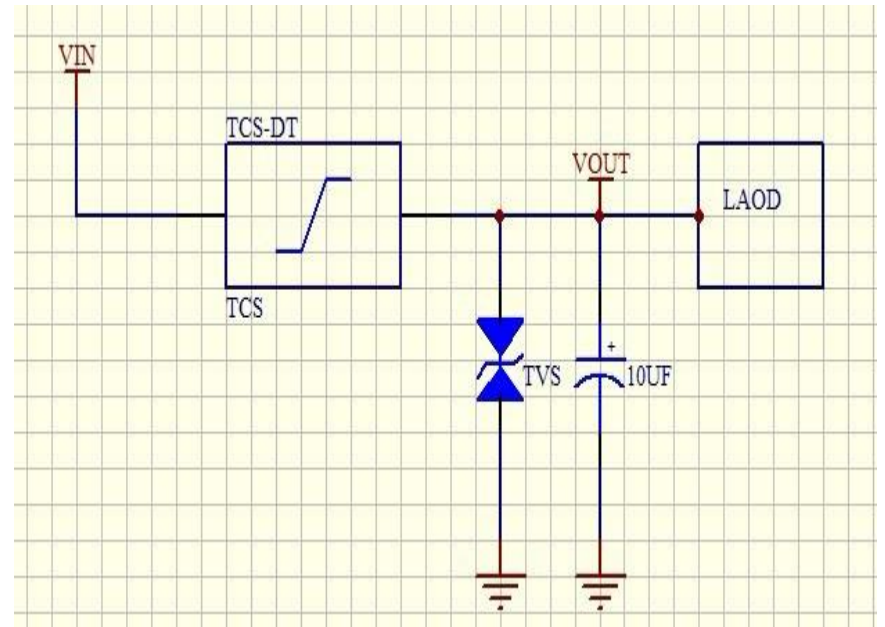

推荐TCS软启动电路

Reference Design for Industrial Applications-3

Pressure Transmitter – HART application

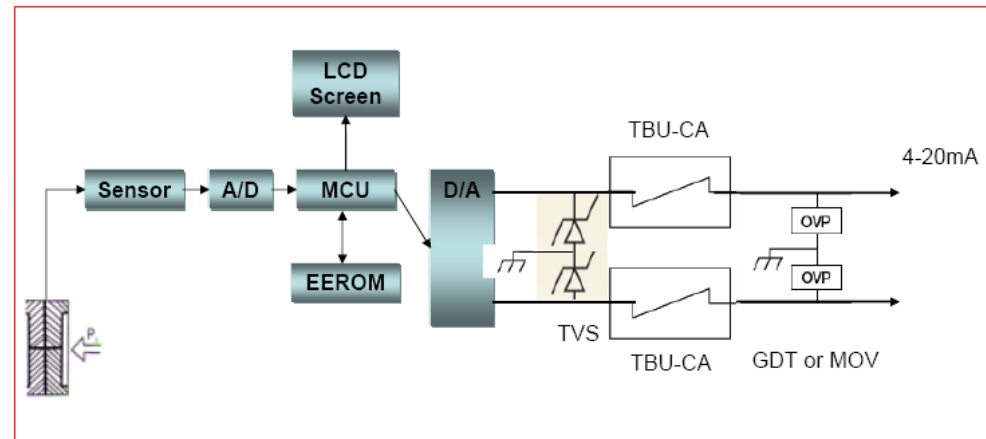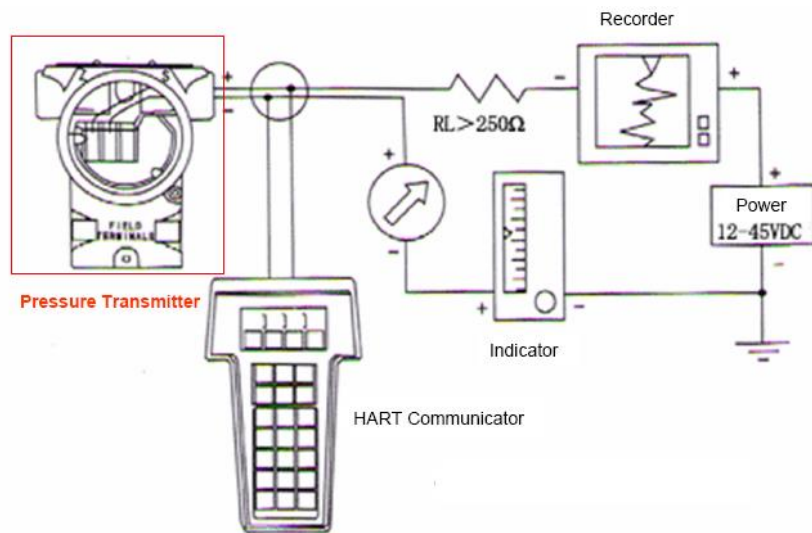

Pressure Transmitter with Transient Protection


- **Port Protection**

- u **GDT: 2027-09-SM or 2026-07**
- u **TBU™: C650-180-WH**
- u **TVS: SMBJ51CA**


Testing standard: GB/T 17626.5 surge standard with 150 V insulation live testing

Solutions - Industrial


RS232 Interface

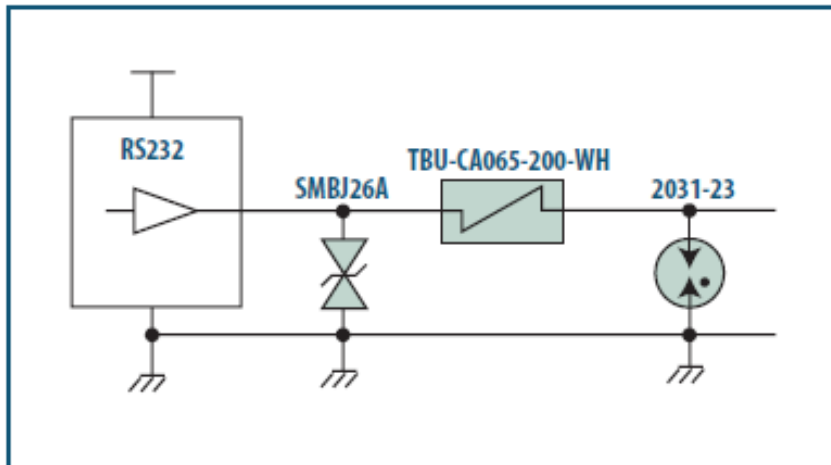


RS485 Interface

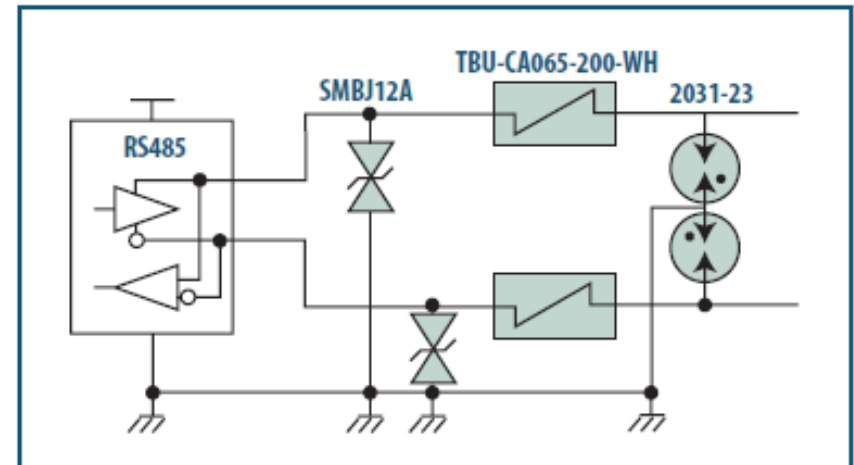

RS422 Interface

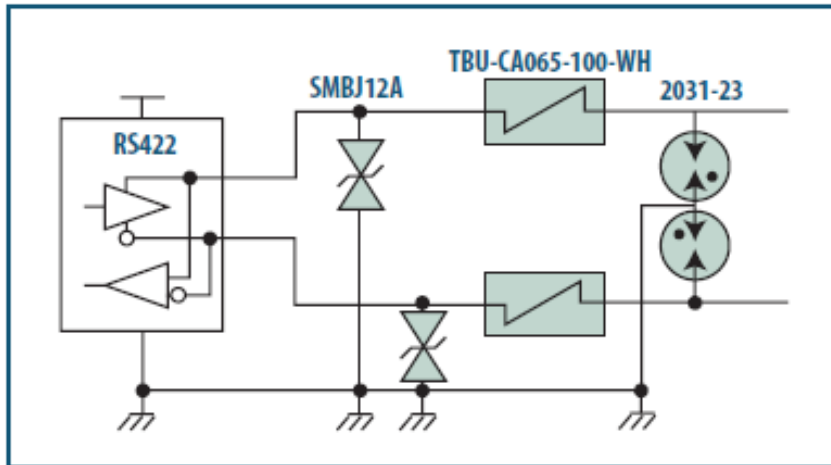


CANBUS

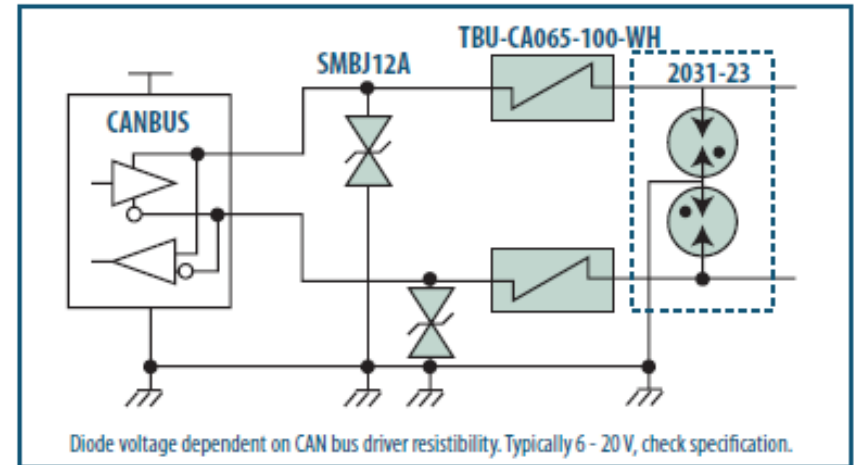


Solutions – Industrial


Intelligent Transport System

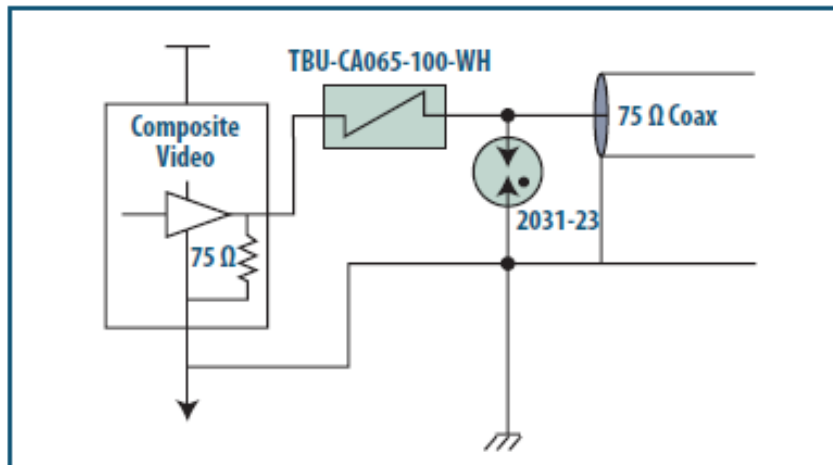


Intrinsically Safe Sensor

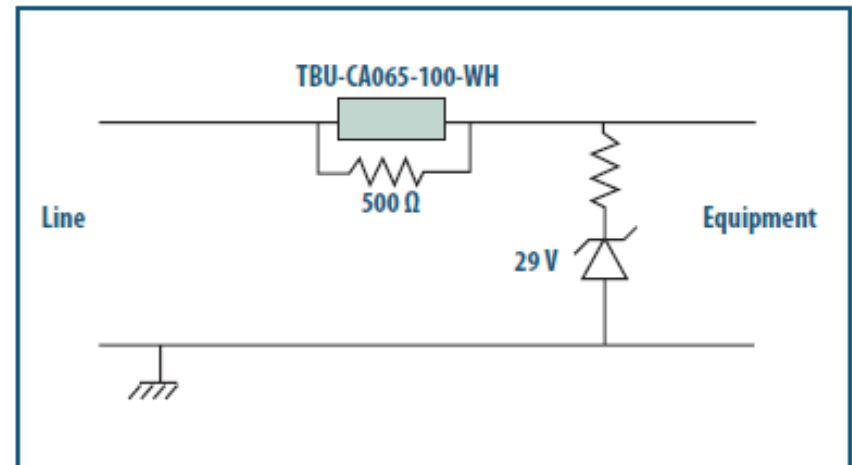

Microwave Link

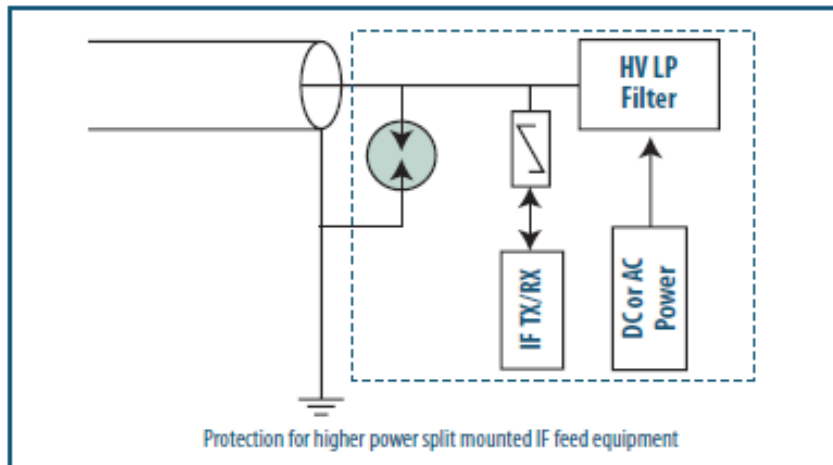


Video Surveillance

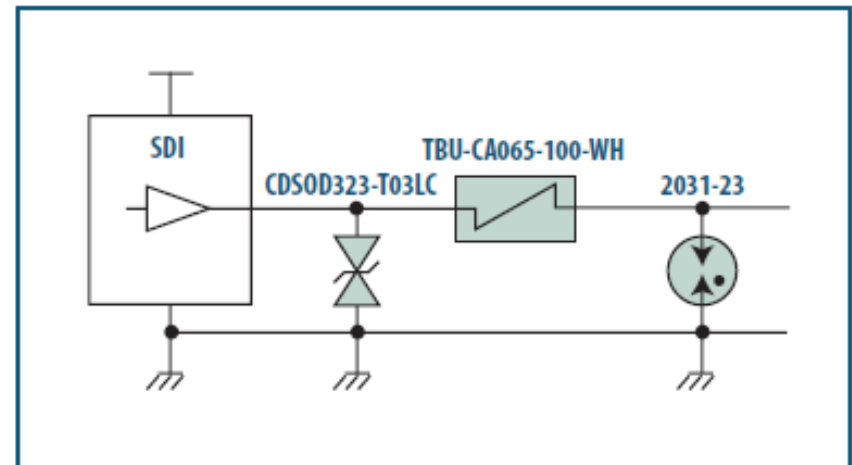


TBU Solution Has Lowest Component Count

Voice Port Protection

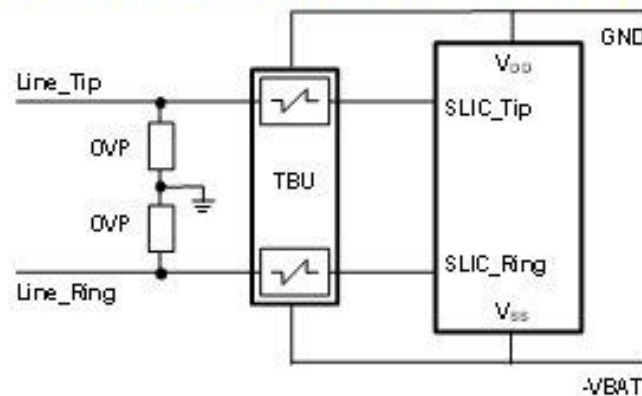

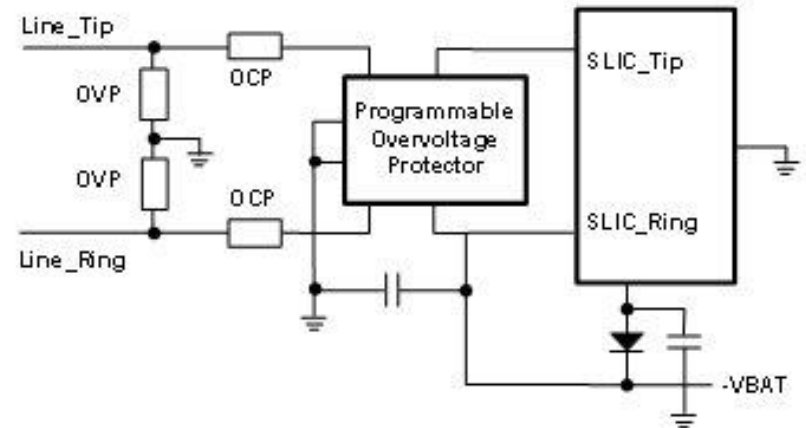- TBU block surge surge and power fault
- Simple, 3 Components
- Meets 4kV and 6kV surge
- Lowest residual voltage
- Tightest line balance
- OVP-GDT, Thyristor, MOV




- Conventional design
- 8 Components
- 4kV require primary protection OVP
- OCP- Fuse, PTC

TBU Solution Has 100X Less Let-Thru Energy


Surge Test: 10/700 μ s, 5000V, 400A

TBU/GDT Protection

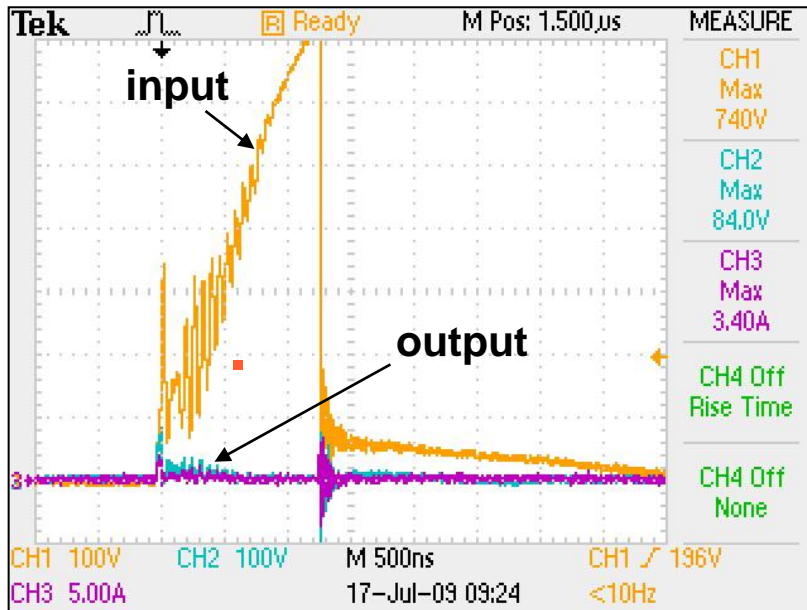

Ch1 – input V (yellow)
Ch2 – output V (blue)
Ch3 – current (purple)

PTC/Thyristor Protection

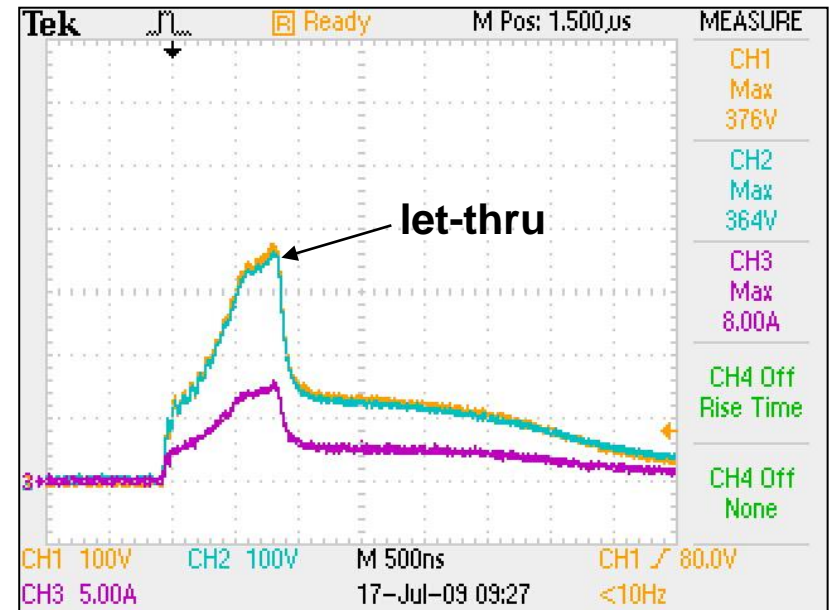

Ch1 – input V (yellow)
Ch2 – output V (blue)
Ch3 – current (purple)

TBU-PL Solution for Voice Port



- Triggers on current or any voltage exceeding the Vbat (-20V to -180V) SLIC :

(i) Enhanced GR-1089 IntraBuilding + 2/10 5kV/500A, ITU K.2x 2kV

PL075-200-WH + 10D201K or 10D391K

(ii) ITU K20/21/45 (10/700 2kV-4kV, 600Vac 600ohms 0.2s induction)

PL085-100-WH+ 2*10D391K

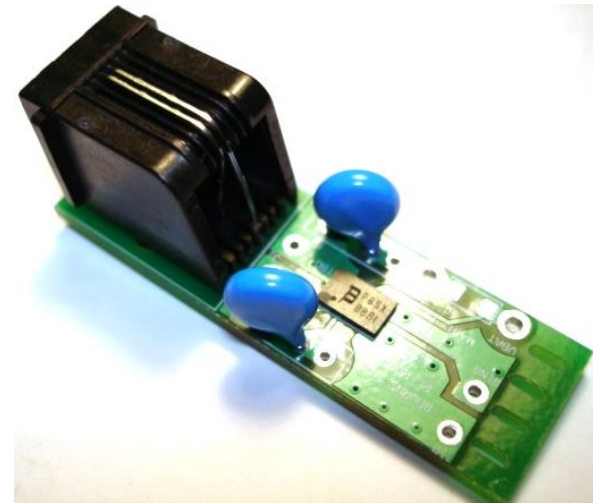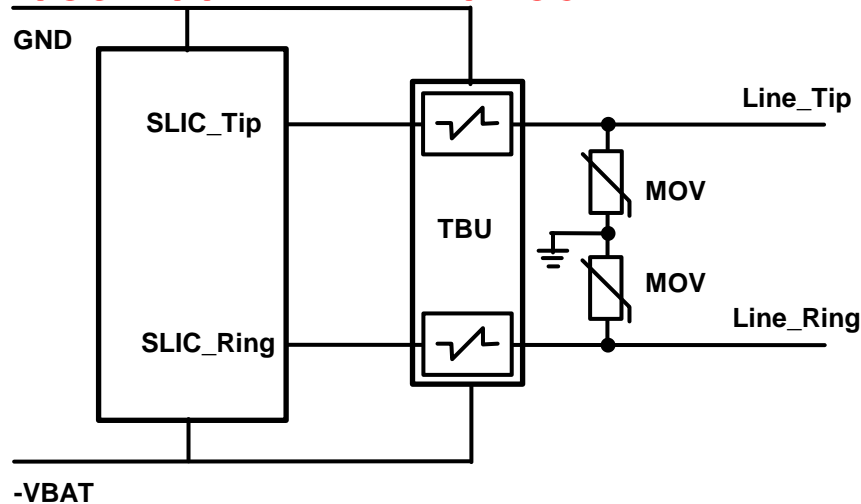

Engineering Tools

- Application notes
- Evaluation boards
- Data sheets
- Lab kits
- FAE support
- Online LED design tool

| Features | | Applications |
|----------------------|----------------------------------|------------------|
| • RoHS Compliant | • 12V, 24V, 48V, 72V, 120V, 240V | • LED drivers |
| • 100% Lead Free | • 12V, 24V, 48V, 72V, 120V, 240V | • LED lighting |
| • 100% Halogen Free | • 12V, 24V, 48V, 72V, 120V, 240V | • LED display |
| • 100% Phosphor Free | • 12V, 24V, 48V, 72V, 120V, 240V | • LED backlights |
| • 100% Silver Free | • 12V, 24V, 48V, 72V, 120V, 240V | • LED indicators |
| • 100% Tin Free | • 12V, 24V, 48V, 72V, 120V, 240V | • LED modules |
| • 100% Copper Free | • 12V, 24V, 48V, 72V, 120V, 240V | • LED arrays |
| • 100% Nickel Free | • 12V, 24V, 48V, 72V, 120V, 240V | • LED strips |
| • 100% Lead Free | • 12V, 24V, 48V, 72V, 120V, 240V | • LED panels |
| • 100% Halogen Free | • 12V, 24V, 48V, 72V, 120V, 240V | • LED tubes |
| • 100% Phosphor Free | • 12V, 24V, 48V, 72V, 120V, 240V | • LED fixtures |
| • 100% Silver Free | • 12V, 24V, 48V, 72V, 120V, 240V | • LED modules |
| • 100% Tin Free | • 12V, 24V, 48V, 72V, 120V, 240V | • LED arrays |
| • 100% Copper Free | • 12V, 24V, 48V, 72V, 120V, 240V | • LED strips |
| • 100% Nickel Free | • 12V, 24V, 48V, 72V, 120V, 240V | • LED panels |
| • 100% Lead Free | • 12V, 24V, 48V, 72V, 120V, 240V | • LED tubes |
| • 100% Halogen Free | • 12V, 24V, 48V, 72V, 120V, 240V | • LED fixtures |

Application Note
Generator Interface Protection

BACKGROUND OF A TYPICAL GENERATOR INSTALLATION

The installation of a generator can be hindered by a variety of people from non-technical to a team of specialists. The role of generator interface protection is to provide a means of protection for the generator and the load it is connected to. The generator interface protection is a device that is connected between the generator and the load. It is designed to protect the generator and the load from damage caused by over-voltage, over-current, and short-circuit conditions.



BOURNS®

ENTER REQUIREMENTS

Power LED

Filter Your Results

Color: All

lo(-): All | 0 >2

Lumi. Flux(>=): All | 0 600

FootPrint(<=): All | 0 500

Configure LED

LED Operating Current: 0.35 A

Part #: Custom

Vforward: 3.5 V

Rdynamic: 0.8 Ω

Or Use Custom LED:

Configure LED Array

Series: 1


Parallel: 1

Vload: 3.5 V

Iload: 0.35 A

Click Below To Select An LED

Click Below To Select An LED

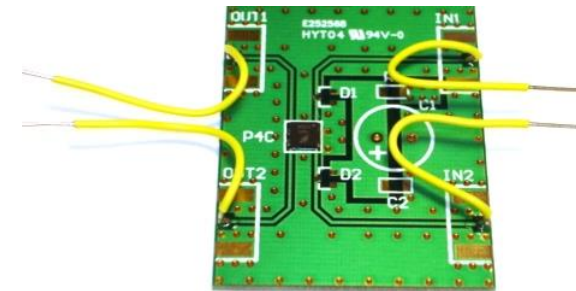

Success Stories using TBU Products

Telecom

Cisco

SLIC Protection

P850-G200-WH

Adtran

Ethernet Protection

P40-G240-WH

Selta Telematica

VDSL Protection

TBU-CA050-500-WH

Industrial

Generac

Generator Controller Protection

C650-260-WH

Catu

Detector Sensor

C850-180-WH

Geotest-Marvin

Temp Sensor Protection

C650-100-WH

Instrumentation

Advantest

ATE Test Point Protection

TBU-CA025-050-WH

Schut Gemometrische

Measure Point Protection

P40-G240-WH

Chuanyi Automation

RS-485 Port Protection

C650-180-WH

Aerospace

Nord-Micro AG

Boeing 787 Air Pressure Control

C650-100-WH

Rockwell Collins


Aircraft Power Circuit Protection

C650-100-WH

TQ Systems

Airbus Cabin Light Protection

C650-260-WH

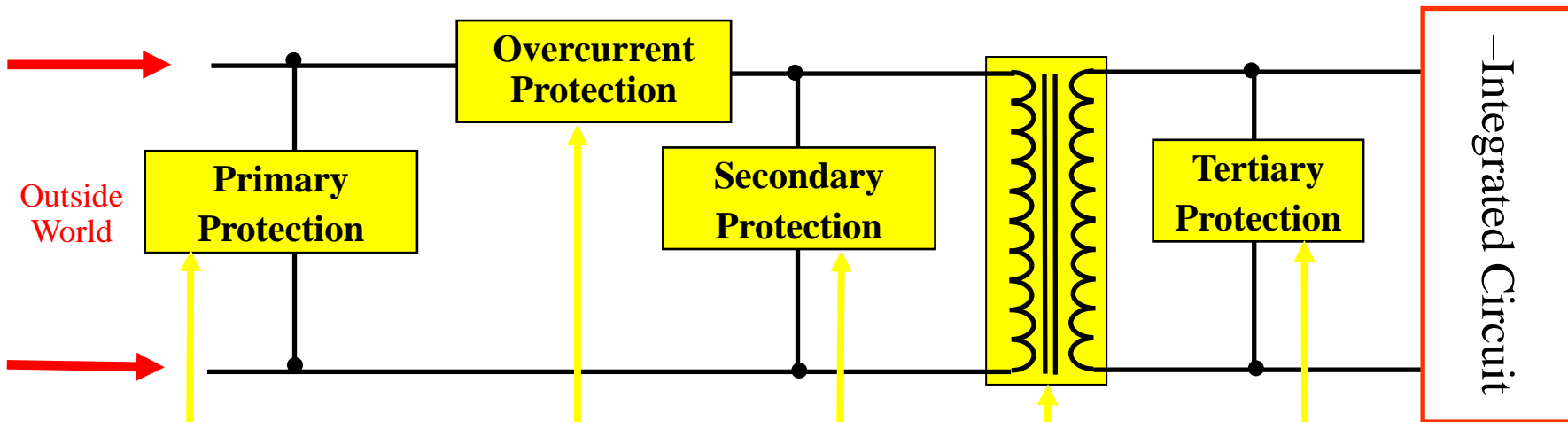

5

Primary (GDT/OSP)

4

PTC Multifuse®

SinglFuse™

Telefuse®

TBU™

Line Feed Resistor

3

TISP®

Fast GDT

3

Transformers

Inductors

1

TVS Diodes

Chipguard™

EMI Filters

STANDARDS